

Analysis and Design Optimisation of Electronic Circuits using Oscad and OpenModelica

OpenModelica Annual Workshop 2015

Rakhi R and Kannan M. Moudgalya
Indian Institute of Technology Bombay, India

February 2, 2015



Outline

- What is Oscad?
- Enhancing explanation feature using OM in Oscad v2.0
- Circuit design optimisation examples
- Integrating Ngspice to Modelica converter in OM suite
- Conclusions and future work




What is Oscad?


- Open Source Electronic Design Automation (EDA) tool
- Developed at IIT Bombay
- Capable of circuit design, simulation, analysis (explanation feature) and PCB layout design
- Runs on Linux, Windows, Aakash
- About half a million students need such a tool every year in India
- India is also a centre for circuit designs



Schematics: Oscad on Aakash

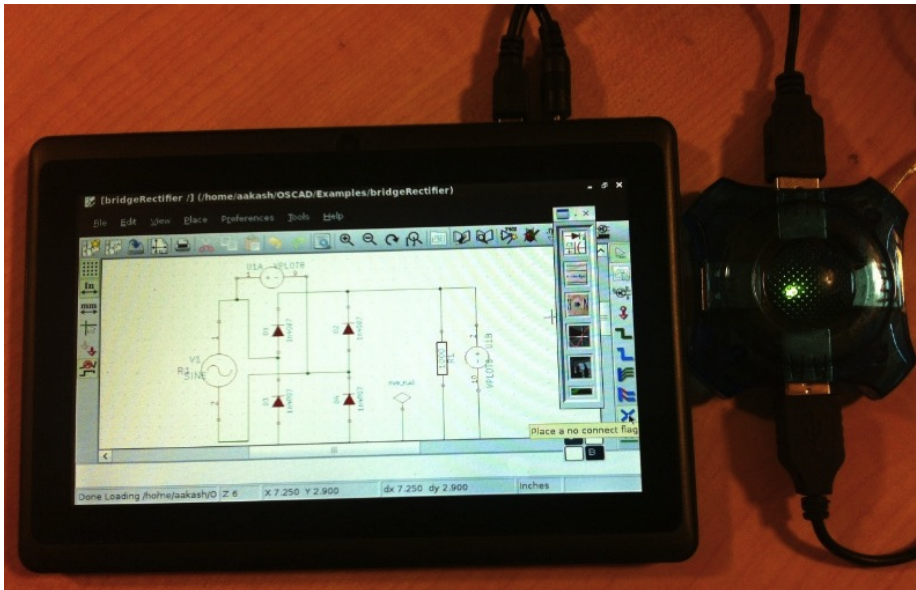


PCB layout: Oscad on Aakash

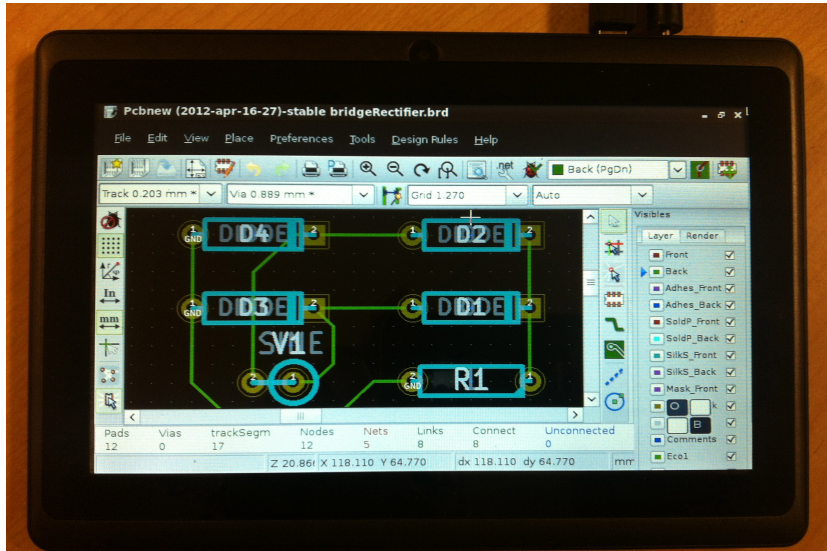

Method to use: Oscad on Aakash



Released Oscad Book as Open Source

 

Oscad: Electronic Design Automation

Built by putting together

- KiCAD for schematics
- Ngspice for simulation
- Fritzing for bread boarding
- Scilab to see mathematical equations
- GHDL for digital simulation




Explanation Facility

- Wanted to extract mathematical equations
- Can explain (oscillations, correctness, etc.) using them
- Previous method: manual generation
- Needed to maintain the interface to solvers
- Needed different interfaces for different types of problems
- Developed an OpenModelica interface



Design Flow in Oscad v2.0

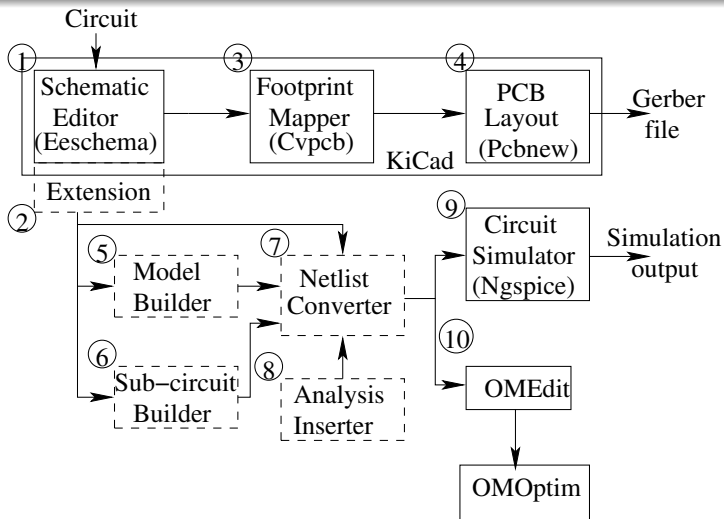

Create circuit schematic → Ngspice netlist → use OM tools for optimisation and circuit equations



Integrating OpenModelica and Oscad

- 1 Convert Ngspice netlist to Modelica code
- 2 \LaTeX interface to display equations in standard mathematical notations
- 3 Open OMOptim for circuit design optimisation




Ngspice to Modelica Conversion


- OM requires circuit description in Modelica language
- Oscad provides circuit description as Ngspice netlist
- Netlist converters available in Dymola, do not work in OM
- A tool for Ngspice to Modelica conversion developed for OM
- Takes care of Spice device parameters, can handle subcircuits
- Opens the converted Modelica code in OMEdit



 Comparison of Ngspice and Modelica for Bridge Rectifier with Filter



Ngspice Simulation

 

OM Simulation



L^AT_EX Interface for Equation Generator



L^AT_EX Interface for Equation Generator


- 1 Ngspice code converter generates Modelica code
- 2 OMC generates equations from Modelica code
- 3 Parser extracts the equations and writes to a text file
- 4 Python code converts text to L^AT_EX
- 5 Compile L^AT_EX code to produce pdf

Shell script to perform all the above steps.

Let us see the output of some of these steps using a voltage divider circuit



 Equation Generator Example: Circuit and Ngspice Netlist



```
r2 2 0 100
r1 2 1 100
v1 1 0 5
.dc v1 0e-00 5e-00
1e-00
* Control State-
ments
.control
run
.endc
.end
```



OpenModelica Description

```
model max_power_transfer
Modelica.Electrical.Analog.Basic.Ground
ground1;
Modelica.Electrical.Analog.Basic.Resistor R1(R
= 100);
Modelica.Electrical.Analog.Basic.Resistor R2(R
= 100);
Modelica.Electrical.Analog.Sources.ConstantVoltage
VDC(V = 5);
equation
connect(VDC.n, ground1.p);
connect(R2.n, ground1.p);
connect(R1.n, R2.p);
connect(VDC.p, R1.p);
end max_power_transfer;
```



Output of Parser

Equations (9, 9)

```
=====
1/1 (1): R2.LossPower = (-R2.v) * VDC.i
2/2 (1): R2.v = (-R2.R_actual) * VDC.i
3/3 (1): R1.v = VDC.V - R2.v
4/4 (1): R1.LossPower = (-R1.v) * VDC.i
5/5 (1): R1.v = (-R1.R_actual) * VDC.i
6/6 (1): R2.R_actual = R2.R * (1.0 + R2.alpha *
7/7 (1): R1.R_actual = R1.R * (1.0 + R1.alpha *
8/8 (1): R1.T = R1.T_ref
9/9 (1): R2.T = R2.T_ref
```

State Sets



```
\begin{align}
R2.LossPower &= (-R2.v) \times VDC.i \\
R2.v &= (-R2.R\_act) \times VDC.i \\
R1.v &= VDC.V - R2.v \\
R1.LossPower &= (-R1.v) \times VDC.i \\
R1.v &= (-R1.R\_act) \times VDC.i \\
R2.R\_act &= R2.R \times (1.0 + R2.alpha \times \\
&\quad \times (R2.T - R2.T\_ref)) \\
R1.R\_act &= R1.R \times (1.0 + R1.alpha \times \\
&\quad \times (R1.T - R1.T\_ref)) \\
R1.T &= R1.T\_ref \\
R2.T &= R2.T\_ref \\
\end{align}
```



Equations Generated

$$R2.LossPower = (-R2.v) \times VDC.i \quad (1)$$

$$R2.v = (-R2.R_{act}) \times VDC.i \quad (2)$$

$$R1.v = VDC.V - R2.v \quad (3)$$

$$R1.LossPower = (-R1.v) \times VDC.i \quad (4)$$

$$R1.v = (-R1.R_{act}) \times VDC.i \quad (5)$$

$$R2.R_{act} = R2.R \times (1.0 + R2.\alpha \times (R2.T - R2.T_{ref})) \quad (6)$$

$$R1.R_{act} = R1.R \times (1.0 + R1.\alpha \times (R1.T - R1.T_{ref})) \quad (7)$$

$$R1.T = R1.T_{ref} \quad (8)$$

$$R2.T = R2.T_{ref} \quad (9)$$



Circuit design optimisation examples




Circuit design optimisation examples

- Inverter chain delay minimisation
- Low noise amplifier design



Min. prop. delay in CMOS inv. chain

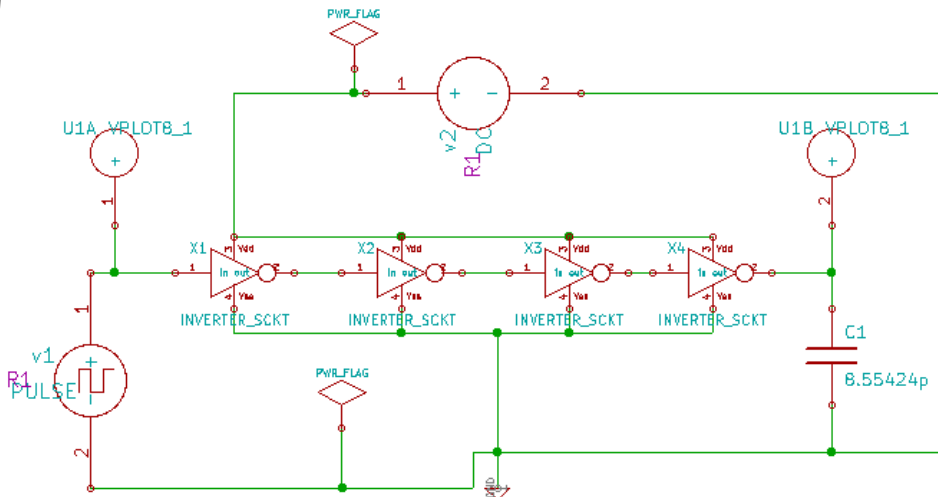

- $0.5\mu\text{m}$ CMOS, Input frequency 500MHz
- In each inverter, NMOS, width $W_n = w_{inv} \times \lambda$, PMOS, $W_p = 3W_n$, $\lambda = 0.25\mu\text{m}$



Parameter optimisation

- Find widths w_{inv2} , w_{inv3} , w_{inv4} such that propagation delay is minimum
- Delay min. when width of every inverter in the chain approx. 4 times that of previous one

Algo.	Delay (s)	w_{inv2} , w_{inv3} , w_{inv4}	Time (m)
PSO	2.73e-10	34.95, 119.21, 463.40	15:47
NSGA2	2.71e-10	36.87, 137.84, 508.16	15:40
SPEA2	2.86e-10	33.44, 149.63, 345.18	17:23

- Widths multiplied by about 3.6 (on an average) in subsequent stages



Parameter optimisation

- Above problem converted to 1 parameter optimisation problem
- Defined $W_{inv2} = h \times W_{inv1}$, $W_{inv3} = h^2 \times W_{inv1}$ so on
- h optimised for minimum delay

Algorithm	Delay (s)	h	Comp. Time (min.)
PSO	2.69e-10	3.9896	15:13
NSGA2	2.69e-10	3.9942	16:10
SPEA2	2.69e-10	4.0020	15:08

- The results clearly show that the delay is minimum when the stage effort is around 4



Parameter optimisation results

2-300iter-OneParam-Real

Optimization (2)


Inv-Chain-PSO-100iter-one-param-final

Inv-chain-SPEA2-100iter-one-param-final

Optimization (2) result

X theDelay

Y w_one_param

 

Clearly shows delay converges to a minimum when stage effort is 4.




Low Noise Amplifier Design for Maximum Gain and Minimum Power

- LNA circuit optimised for max gain, min power consumption, with sufficient linearity
- Designed for min Noise Factor
- Resonant frequency $\omega_0 \approx 10^{10} \text{s}^{-1}$
- Input impedance, $R_s = 50\Omega$
- Cascode Common Source (CS) LNA with inductive degeneration used
- $0.5\mu\text{m}$ CMOS technology



LNA Optimisation Problem

 

Max. Gain, Min. Power,
subject to

$$V_{gs1} > V_{th}$$

$$V_{ds1} > V_{dsat}$$

$$V_{gs2} > V_{th}$$

$$V_{ds2} > V_{dsat}$$

$$I_{ds} \geq 0.0015A$$

$$0.98\omega_0 \leq f_{out} \leq 1.02\omega_0$$

V_{gs_i} , V_{ds_i} : Voltages of gate-source, MOS Mn_i 's drain-source
 V_{th} : Threshold voltage, I_{ds} : Drain-source current



Optimisation Results

Parameter	Value
L2	7.136nH
C2	1.396pF
w_{nbias}	236λ
$w_{M2,M3}$	2360λ
R2	9.383k Ω
R3	2.63k Ω
NF	2.08
power	10.63mW
gain	9.3

- Performed multi objective optimisation using PSO algorithm
- Output freq: 9.96×10^{10} rad/s, within limits




Integrating Ngspice to Modelica Converter



Integrating Ngspice to Modelica Converter

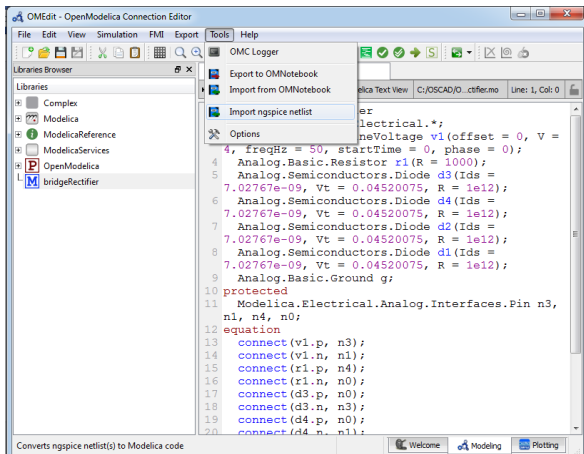- API `ngspicetoModelica()` added to `omc`
- Tool “Import Ngspice Netlist” added in OMEdit
- Generates Modelica code and opens in OMEdit



The screenshot shows the OMEdit - OpenModelica Connection Editor interface. The 'Tools' menu is open, highlighting 'Import ngspice netlist'. The main text area contains the following Modelica code:

```
1 electrical.*;  
2 sineVoltage v1(offset = 0, v =  
3 4, freqHz = 50, startTime = 0, phase = 0);  
4 Analog.Basic.Resistor r1(R = 1000);  
5 Analog.Semiconductors.Diode d3(Ids =  
6 7.02767e-09, Vt = 0.04520075, R = 1e12);  
7 Analog.Semiconductors.Diode d4(Ids =  
8 7.02767e-09, Vt = 0.04520075, R = 1e12);  
9 Analog.Semiconductors.Diode d2(Ids =  
10 7.02767e-09, Vt = 0.04520075, R = 1e12);  
11 Analog.Semiconductors.Diode d1(Ids =  
12 7.02767e-09, Vt = 0.04520075, R = 1e12);  
13 Analog.Basic.Ground g;  
14 protected  
15 Modelica.Electrical.Analog.Interfaces.Pin n3,  
16 n1, n4, n0;  
17 equation  
18 connect(v1.p, n3);  
19 connect(v1.n, n1);  
20 connect(r1.p, n4);  
21 connect(r1.n, n0);  
22 connect(d3.p, n0);  
23 connect(d3.n, n3);  
24 connect(d4.p, n0);  
25 connect(d4.n, n1);
```



Conclusions

- Explanation feature in Oscad enhanced using OM tools
- Feature helps user gain more insights into the circuit
- Design optimisation facility helps design efficient circuits in a short time
- Implemented \LaTeX interface to equation generator in OM
- A generic Ngspice netlist to Modelica code converter added in OM suite
- Helps obtain Modelica code from Ngspice netlists, without creating schematic in Oscad
- Several optimisation problems illustrated using enhanced explanation feature in Oscad 2.0



Thanks

kannan@iitb.ac.in

